
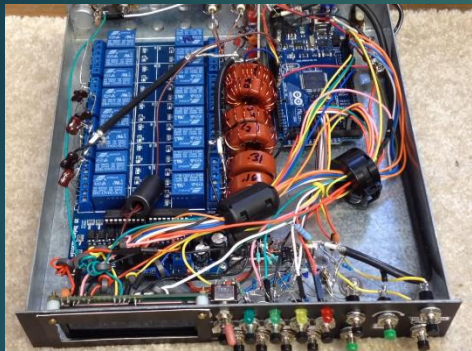



Automatic Antenna Tuners

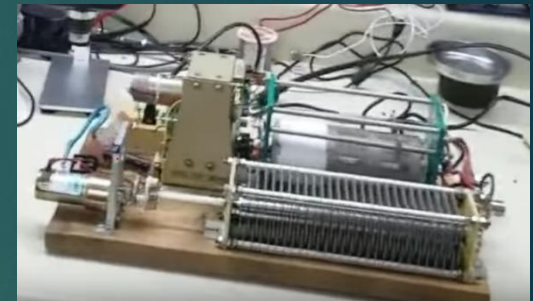

DWAYNE KINCAID
WD8OYG




What is an Antenna Tuner?

- ▶ Anything called a tuner, coupler, matchbox, transmatch, ATU, etc
- ▶ Adjustable impedance transformer that goes between the radio and antenna
- ▶ Helps provide maximum power transfer from radio to antenna system
- ▶ Makes the radio happy! 

And why do I need one?

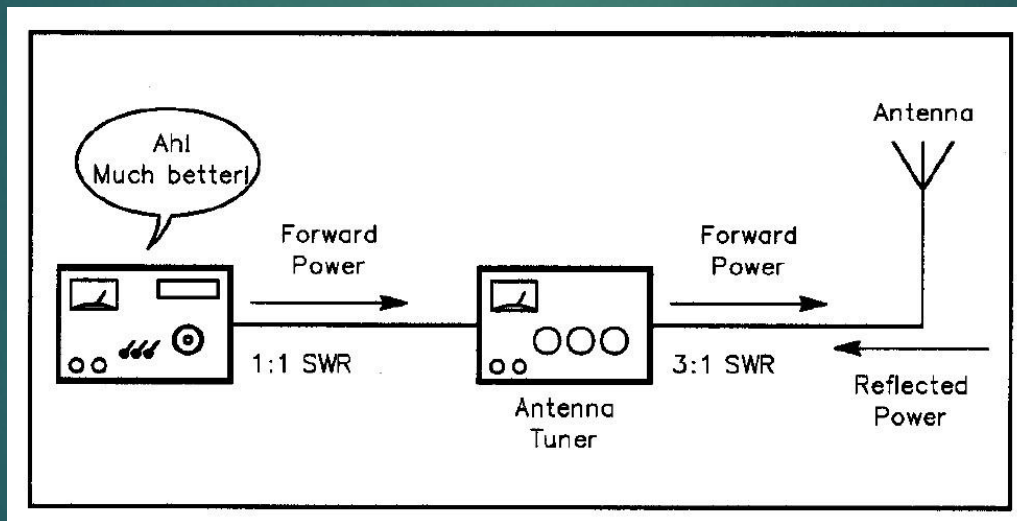- ▶ An antenna tuner transforms the impedance of an antenna and/or feed line to a value (50 ohms) so that the transceiver can produce the maximum amount of RF power.



A History of Tuners

- ▶ Started as fixed matching networks Add a capacitor or inductor someplace to get the light-bulb to be the brightest.
- ▶ Variable networks became popular with the Johnson KW Matchbox 1950s
- ▶ Autotuners were available in the early 90's. SGC Kenwood
- ▶ AT-11 Desktop in 1996 QST



Three Types of Autotuners

- ▶ Inside the radio. Miniature motors or relays. Limited tuning range. Can't measure SWR or RF watts externally.
- ▶ Long wire. Wide tuning range up to 50:1. Weatherproof. Heavy. Expensive. Control Cables.
- ▶ Desktop. Most popular since the 90's. 10:1 range. Scalable from 5 to 1000 watts.




Tuner Location



- ▶ If you use a Variable Matching Device, putting it closer to the feed point is more efficient
- ▶ Coax loss becomes more noticeable above 30 MHz, with SWR above 10:1, or for lengths above 150 feet
- ▶ It's more convenient to have the tuner on the desktop. Laziness usually wins!


The Switched “L” Network

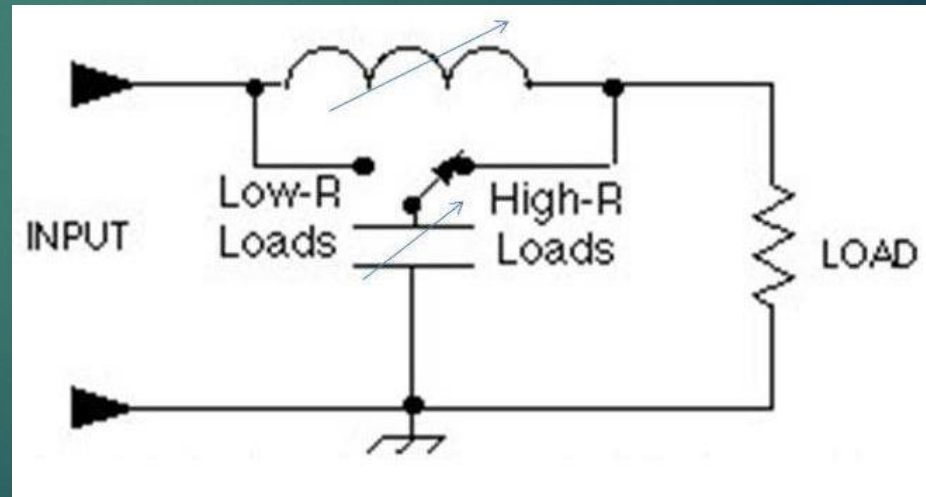- ▶ Transforms $R + jX$ to 50 ohms ($50 + j0$)
- ▶ Good 10 to 1 tuning range
- ▶ Only needs SWR
- ▶ Has single solution
- ▶ Conjugate Match
- ▶ 30% less parts



Hi and Lo-Z

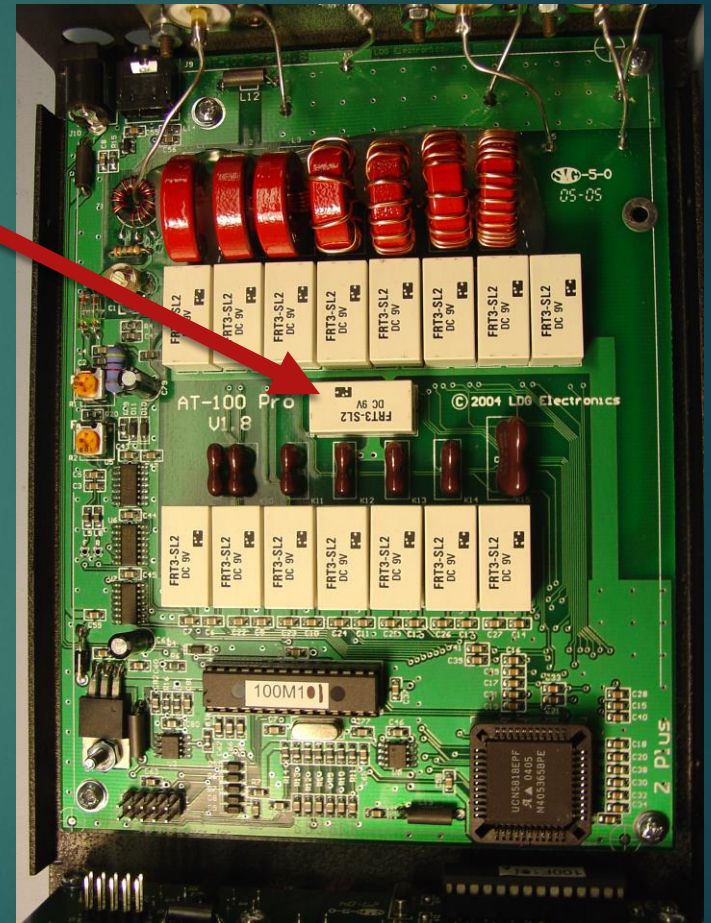- ▶ Software is used to detect if the antenna is High-impedance or Low-Z. Configures capacitor to input or output.
- ▶ When antenna is over 50 ohms, the antenna is Hi-impedance. Capacitor is on antenna side.
- ▶ When antenna is under 50 ohms, it's Lo-Z. Capacitor is on radio side.




Measuring SWR

- ▶ Simple Bruene SWR detector gives Forward and Reverse power
- ▶ Then use Math to get SWR
- ▶ Don't forget, Minimum SWR = maximum power transfer for the single-solution Switched-L Network

$$VSWR = \frac{1 + \sqrt{\frac{\text{REFLECTED POWER}}{\text{FORWARD POWER}}}}{1 - \sqrt{\frac{\text{REFLECTED POWER}}{\text{FORWARD POWER}}}}$$

Adding Power

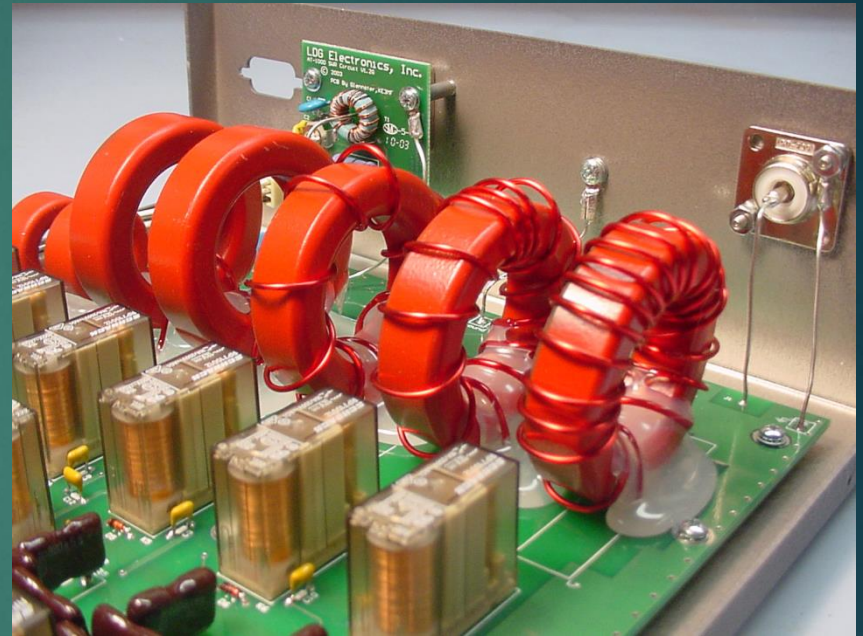- ▶ Capacitor Voltage
 - ▶ 100 watts = 500V
 - ▶ 1000 watts = 2500V
- ▶ Upper limit is 16A relays
- ▶ Inductors Get Bigger




Speed

- ▶ Limited by relay de-bounce time
- ▶ 10 mSec per setting modified Bubble-Sort
- ▶ Up to 300 settings for a tune (3 Seconds)
 - ▶ 10 for Hi/Lo-Z
 - ▶ 100 for Inductors
 - ▶ 100 for Caps
 - ▶ 25 for fine tuning
- ▶ 3 settings for a memory tune (<100 mSec)



Automating it All

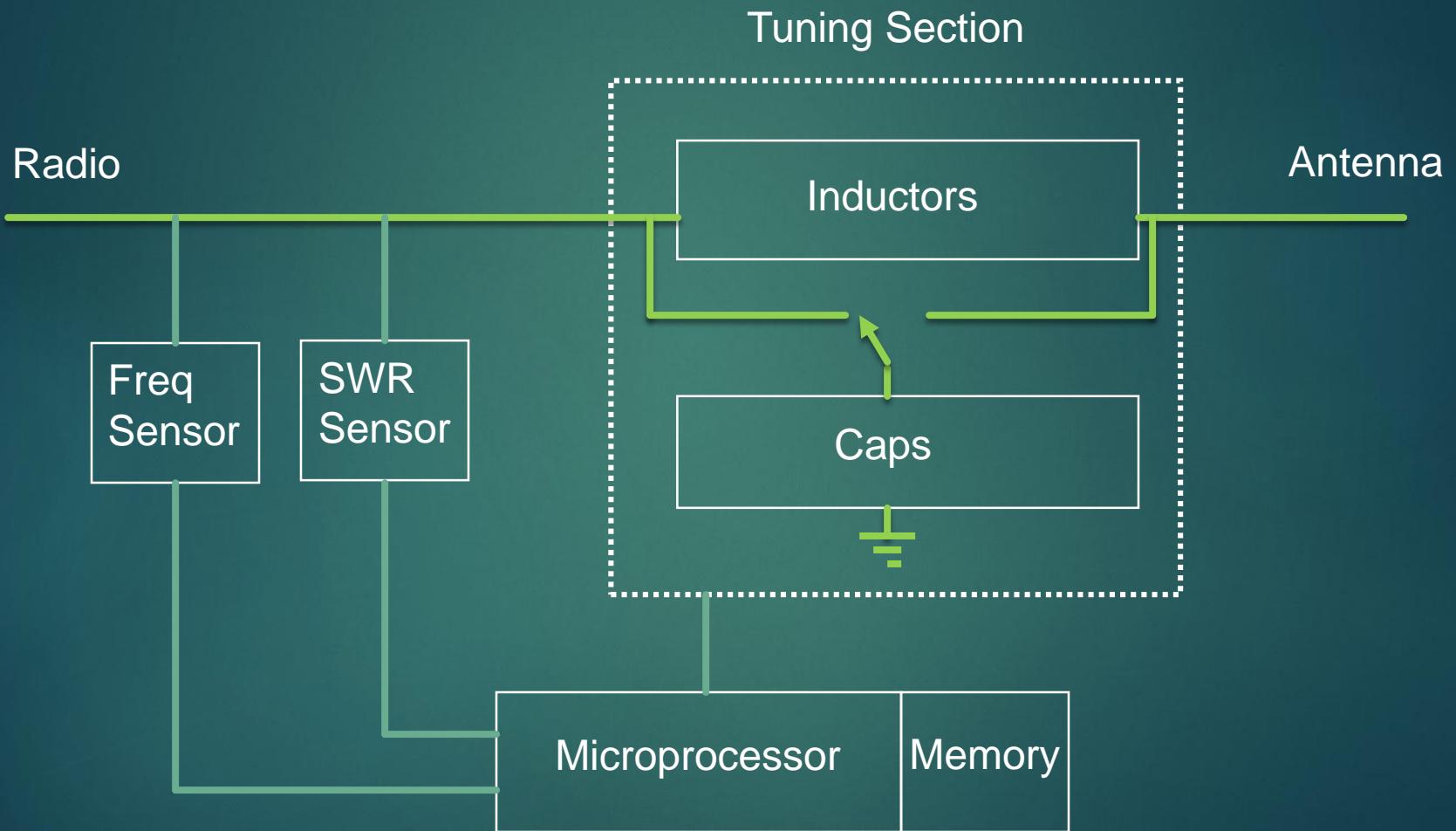

Future



- ▶ Wider desktop tuning range 15:1
- ▶ Better sensor array
- ▶ Analog meters for RF and SWR
- ▶ USB interface for remote operation
- ▶ Simple Operation (Mind reading option)

Sources

- ▶ ARRL Antenna Book
- ▶ <http://www.ab4oj.com/atu/main.html>
- ▶ <http://fermi.la.asu.edu/w9cf/index.html>
- ▶ https://en.wikipedia.org/wiki/Antenna_tuner
- ▶ Alan Wolke W2AEW <https://www.qsl.net/w2aew/>
- ▶ W5KUB Show <https://www.w5kub.com>